

# IMPLEMENTATION OF BOOLEAN LOGIC IN ASSEMBLY

P.PAVAN KUMAR

padmanabhunipavna0@gmail.com

FWC22088

IITH Future Wireless Communication (FWC)

ASSIGN-1

## Contents

<b>1 Components</b>	<b>1</b>
<b>2 Implementation</b>	<b>1</b>
2.1 METHOD-1 . . . . .	1
2.2 METHOD-2 . . . . .	1

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Table-1

## Abstract

To Obtain the Boolean Expression for the Logic circuit shown below

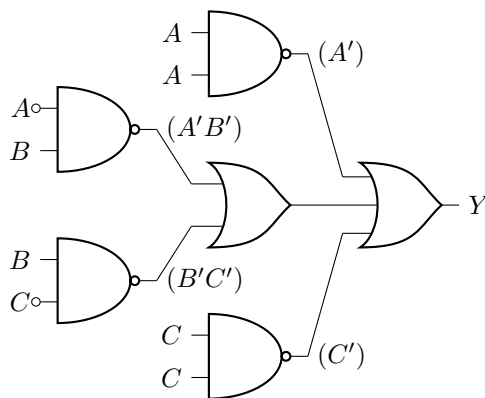


Fig. 1( $Y = A'B' + B'C' + A' + C'$ )

## 2.2 METHOD-2

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	1	1	1	1
	1	1	0	0	1

Fig. 2

**Karnugh Map :** The expression in (2.1) can be minimized using the K-map in Fig 2. In Fig.2 ,the implicants in boxes 0,1,2,3 result in  $A'$  The implicants in boxes 0,4,2,6 result in  $C'$  Thus, after minimization using Fig. 2, (2.1) can be expressed as  $Y = A' + C'$ .....(2.2). Verify the truth table for Y in TABLE 1. The code below realizes the Boolean logic for F in 2.2

<https://github.com/SkocKwOR/FWC-/blob/main/assignment2/ass2/ass2.asm>

## 1 Components

Components	Values	Quantity
Arduino	UNO	1
JumperWires	M-M	5
Breadboard		1

## 2 Implementation

### 2.1 METHOD-1

The truth table for Fig. 1 is available in Table-1 Using Boolean logic, output Y in Table 1 can be expressed in terms of the inputs A, B, C as  $Y = A'B' + B'C' + A' + C'$  .....(2.1) D3,D4,D5 Pins of Arduino are configured as input pins instead of initializing A,B,C inside software,inputs are given manually as A,B,C.led will glow based on Y satisfying the Table-1 The code below realizes the Boolean logic for Y in Table-1

<https://github.com/SkocKwOR/FWC-/blob/main/assignment2/ass1/ass.asm>